

## Lab Project 4

### Lab Goals:

For Lab #4, we will be adding to the functionality of the processor we began creating in Lab #3. Upon completion of this lab, our processor will include support for a program counter, the register file, and control, as well as the features designed in Lab #3.

### Beta vs. Standard MIPS Processor:

Basically, the Beta processor supports fewer instructions. The most significant missing functionality is jumping. Without the ability to jump, we cannot do jumps, branch if equal, branch if not equal, and a whole host of other jump instructions.

### Program Counter:

In order to create the program counter, the ALU from Lab #3 is used. We import the instruction, and then add 4 to it. However, if the control signal reset is selected, we reset the instruction memory to 0x0. This is done by creating 32 2 to 1 multiplexers.


```
.subckt pc clk reset ia[31:0]

  Xxor_b 0#29 VDD 0#2 ia[31:0] xorOUT_b[31:0] xor2
  Xxor_c xorOUT_b[31:0] Cout[30:0] 0 OUT[31:0] xor2
  Xand_a xorOUT_b[31:0] Cout[30:0] 0 andOUT_a[31:0] and2
  Xand_b 0#29 VDD 0#2 ia[31:0] andOUT_b[31:0] and2
  Xor andOUT_a[31:0] andOUT_b[31:0] Cout[31:0] or2
  Xpc_a reset#32 OUT[31:0] 0#32 ia_tmp[31:0] mux2
```

```

Xpc_b ia_tmp[31:0] CLK#32 ia[31:0] dreg
.ends

```

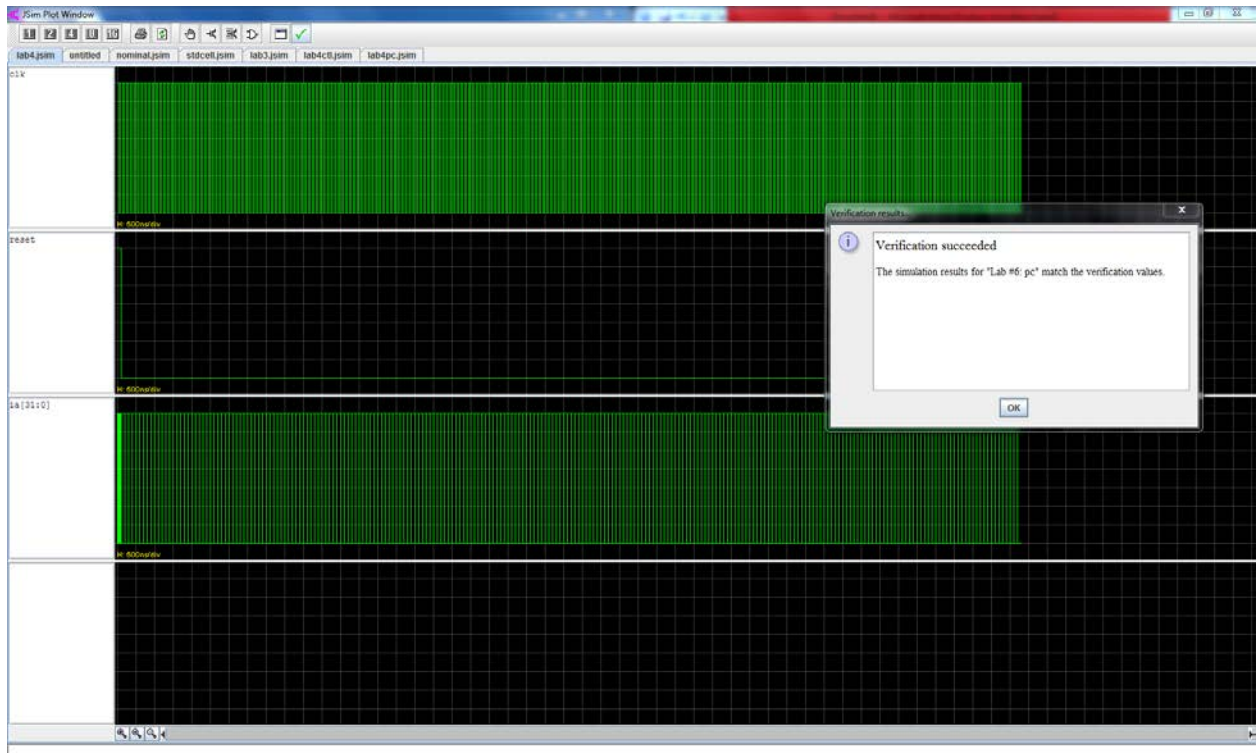

## Register File:

To create the register file, there are 3 signals: ra, rb, and rc. However, because there are only 2 inputs, A mux needs to be used to select between rb and rc, with ra2sel used as the select. Also, the read timing for the \$zero register can be decreased by a hardwiring the data of a \$zero register. Because the \$zero register is a constant, 0, we can directly map the data 0 to the \$zero register address.

```

.subckt regfile clk werf ra2sel ra[4:0] rb[4:0] rc[4:0]
+ wdata[31:0] radata[31:0] rbdata[31:0]

Xregfile

```

```

+ vdd 0 0 ra[4:0] adata[31:0]          // A read port
+ vdd 0 0 ra2mux[4:0] bdata[31:0]      // B read port
+ 0 clk werf rc[4:0] wdata[31:0]      // write port
+ $memory width=32 nlocations=32

```

```
Xrb_mux ra2sel#5 rb[4:0] rc[4:0] ra2mux[4:0] mux2
```

```
Xzilch_and_a ra[3:0] zilch_OUT_a and4
```

```
Xzilch_and_b zilch_OUT_a ra[4] zilch_OUT_b and2
```


```
Xzilch_mux zilch_OUT_b#32 adata[31:0] 0#32 radata[31:0] mux2
```

```
Xzilch_and_ba ra2mux[3:0] zilch_OUT_ba and4
```

```
Xzilch_and_bb zilch_OUT_ba ra2mux[4] zilch_OUT_bb and2
```

```
Xzilch_muxb zilch_OUT_bb#32 bdata[31:0] 0#32 rbdata[31:0] mux2
```

.ends

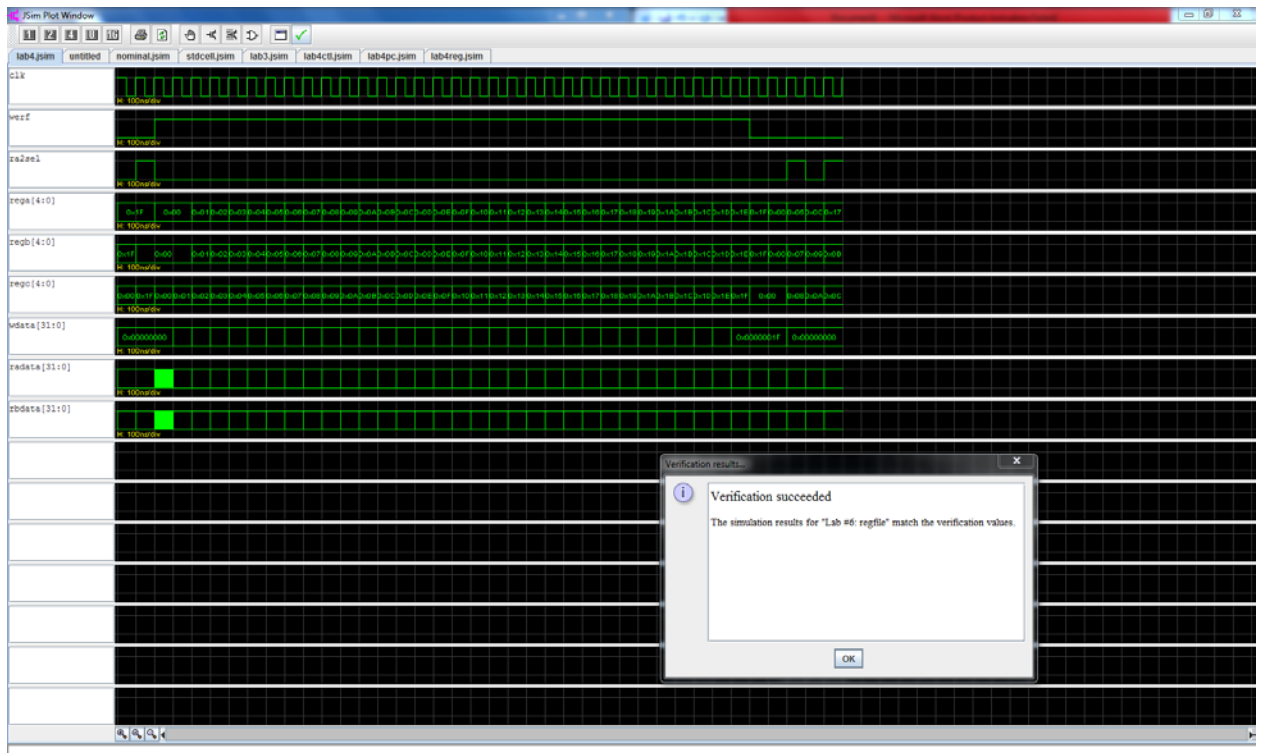

Control:



```
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b000000110000000010 // 011 000
+ 0b00010110000000100 // 011 001
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b000000001000000010 // 100 000
+ 0b00000000100001010 // 100 001
+ 0b00000000000000000000
+ 0b00000000000000000000
+ 0b00000000100101010 // 100 100
+ 0b00000000100111010 // 100 101
+ 0b00000000101101010 // 100 110
+ 0b00000000000000000000
+ 0b00000000111000010 // 101 000
+ 0b00000000111110010 // 101 001
+ 0b00000000110110010 // 101 010
```

```

+ 0b00000000111001010 // 101 011
+ 0b00000000101000010 // 101 100
+ 0b00000000101001010 // 101 101
+ 0b00000000101011010 // 101 110
+ 0b00000000000000000
+ 0b00000010100000010 // 110 000
+ 0b00000010100001010 // 110 001
+ 0b00000000000000000
+ 0b00000000000000000
+ 0b00000010100101010 // 110 100
+ 0b00000010100111010 // 110 101
+ 0b00000010101101010 // 110 110
+ 0b00000000000000000
+ 0b00000010111000010 // 111 000
+ 0b0000001011110010 // 111 001
+ 0b00000010110110010 // 111 010
+ 0b00000010111001010 // 111 011
+ 0b00000010101000010 // 111 100
+ 0b00000010101001010 // 111 101
+ 0b00000010101011010 // 111 110
+ 0b00000000000000000
+ )

```


```

Xxor_moe_a id[31] VDD moeOUT_a xor2
Xxor_moe_b id[30] 0 moeOUT_b xor2
Xxor_moe_c id[29] 0 moeOUT_c xor2
Xxor_moe_d id[28] VDD moeOUT_d xor2
Xxor_moe_e id[27] VDD moeOUT_e xor2
Xxor_moe_f id[26] VDD moeOUT_f xor2
Xmoe_a moeOUT_a moeOUT_b moeOUT_c moeOUT_d moeOUT_g and4

```

```
Xmoe_b moeOUT_g moeOUT_e moeOUT_f VDD moe and4
```

```
.ends
```

 

Beta:

Unfortunately, I was unable to tie all my components together. I tied the program counter and register file together, but could not include the control logic. My error resided in the “ma” register, which I used a buffer with my ALU output.

```
.subckt beta clk reset ia[31:0] id[31:0] ma[31:0] moe mrd[31:0] wr
+ mwd[31:0]
```

```
* PC *
```

```
Xpc clk reset ia[31:0] pc
```

```
* CONTROL *
```

```

Xctl reset id[31:26] ra2sel bsel alufn[4:0] wdsel[1:0] werf
    + moe wr ctl

* REG FILE *

Xbuffer_a id[15:0] id_dummy[15:0] buffer
Xbuffer_b id[15]#16 id_dummy[31:16] buffer
Xmux_a bsel#32 id_dummy[31:0] rbddata[31:0] b[31:0] mux2
Xalu alufn[4:0] radata[31:0] b[31:0] out[31:0] z v n alu
Xmux_b wdsel[0]#32 wdsel[1]#32 0#32 out[31:0] mrd[31:0] 0#32
wdata[31:0] mux4

Xregfile clk werf ra2sel id[20:16] id[15:11] id[25:21]
    + wdata[31:0] radata[31:0] rbddata[31:0] regfile

* RANDOM *

Xbuffer_c rbddata[31:0] mwd[31:0] buffer
Xbuffer_d out[31:0] ma[31:0] buffer

.ends

```



